

# HKUST Dual Program 2019

Level 1 (Engineering – Robotics)


Basic Electronics, Energy and Power

Dr. Tim, Kam-tim WOO ([eetim@ust.hk](mailto:eetim@ust.hk)) and Fox WU ([eefox@ust.hk](mailto:eefox@ust.hk))

# Circuit theory in Mathematics

- Consider two typical circuits, Parallel and Series configuration


Parallel Configuration

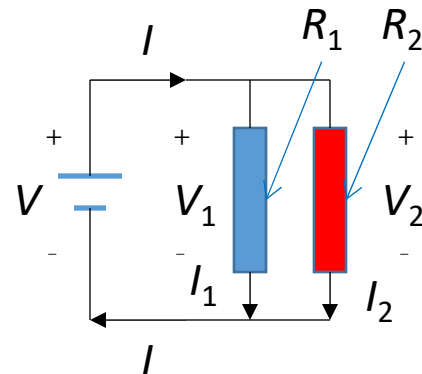

Identities:

$$\begin{aligned} V &= V_1 \\ &= V_2 \\ I &= I_1 + I_2 \\ V_1 &= I_1 R_1 \\ V_2 &= I_2 R_2 \end{aligned}$$

Series Configuration

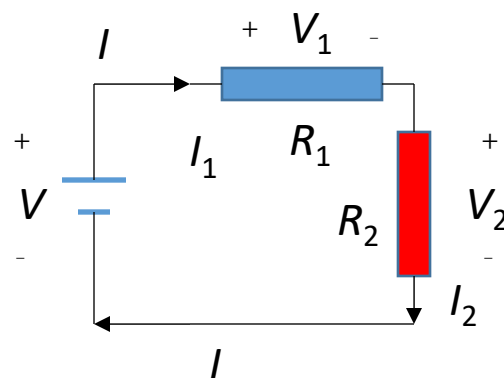


Identities:

$$\begin{aligned} V &= V_1 + V_2 \\ I &= I_1 = I_2 \\ V_1 &= I_1 R_1 \\ V_2 &= I_2 R_2 \end{aligned}$$

# Circuit theory in Mathematics

- Consider Series configuration

Series Configuration

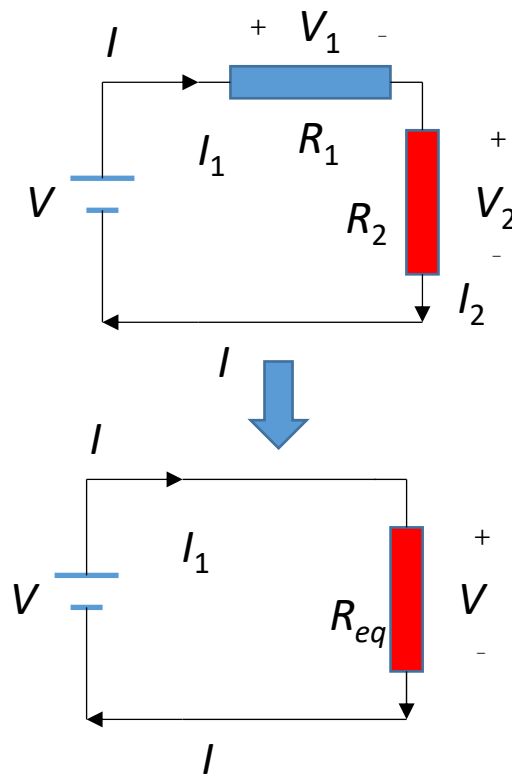


Identities:


$$\begin{aligned} V &= V_1 + V_2 \\ I &= I_1 = I_2 \\ V_1 &= I_1 R_1 \\ V_2 &= I_2 R_2 \end{aligned}$$

$$\begin{aligned} V &= V_1 + V_2 = IR_1 + IR_2 \\ IR_{eq} &= I(R_1 + R_2) \\ R_{eq} &= (R_1 + R_2) \end{aligned}$$

# Series

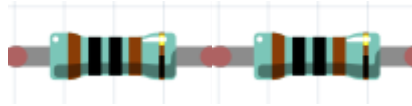

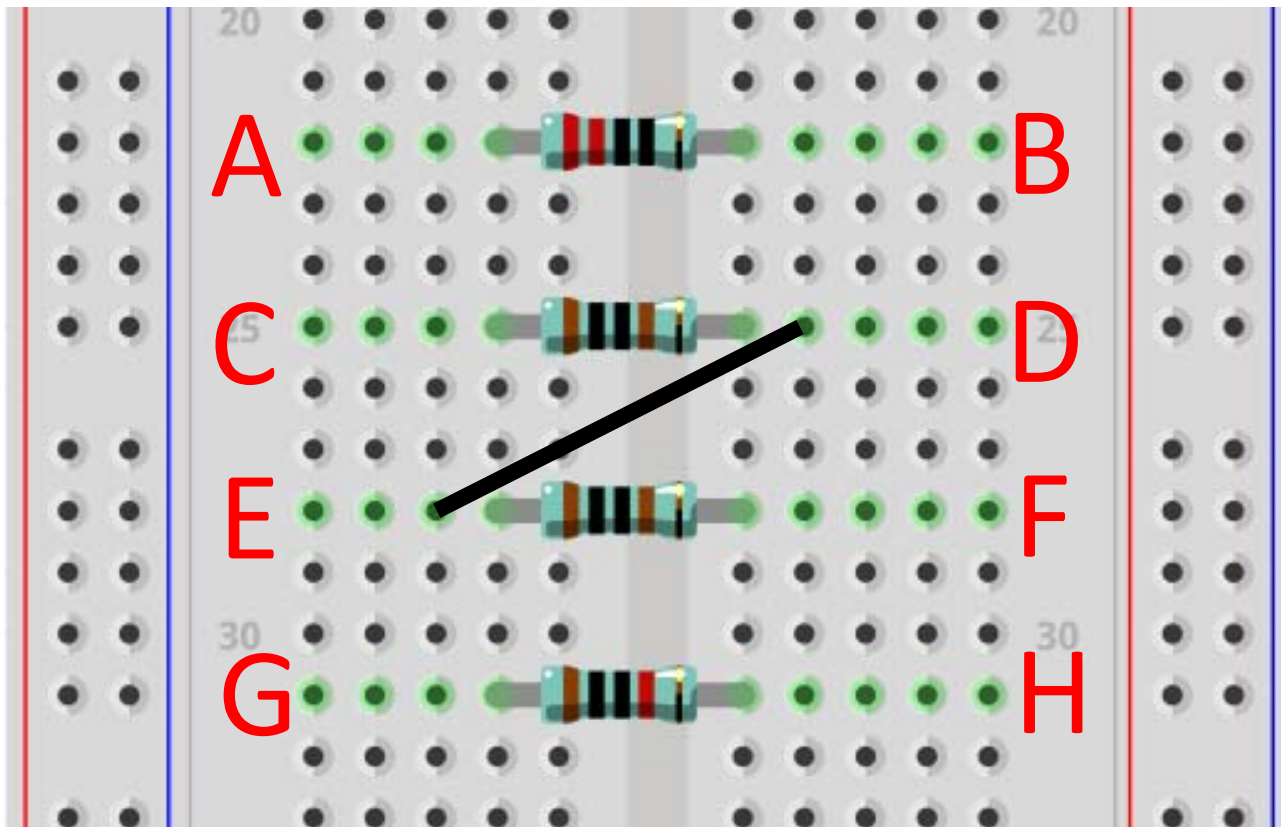
- The 2 middle  $1k\Omega$  resistors are said to be in Series



# Circuit theory in Mathematics

- Parallel configuration


Parallel Configuration

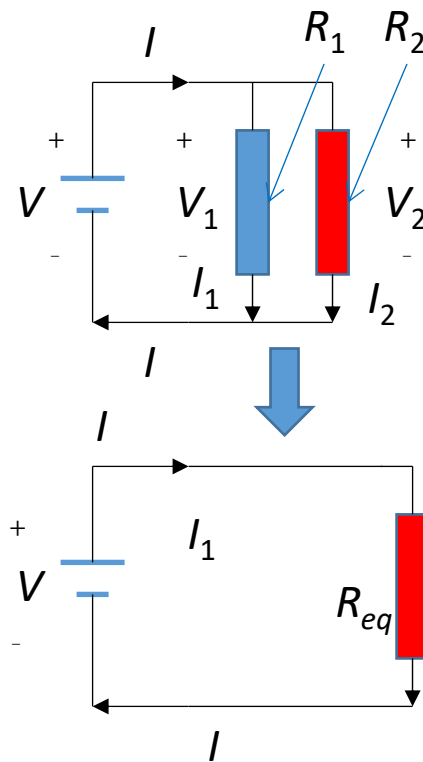


$$\begin{aligned} V &= V_1 \\ &= V_2 \\ I &= I_1 + I_2 \\ V_1 &= I_1 R_1 \\ V_2 &= I_2 R_2 \end{aligned}$$

$$\begin{aligned} I &= I_1 + I_2 = \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V}{R_1} + \frac{V}{R_2} \\ &= \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V \\ I &= \left( \frac{1}{R_1} + \frac{1}{R_2} \right) I R_{eq} \\ \frac{1}{R_{eq}} &= \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \end{aligned}$$

# Parallel

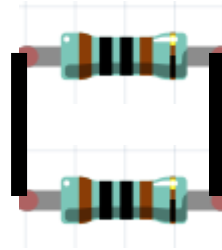

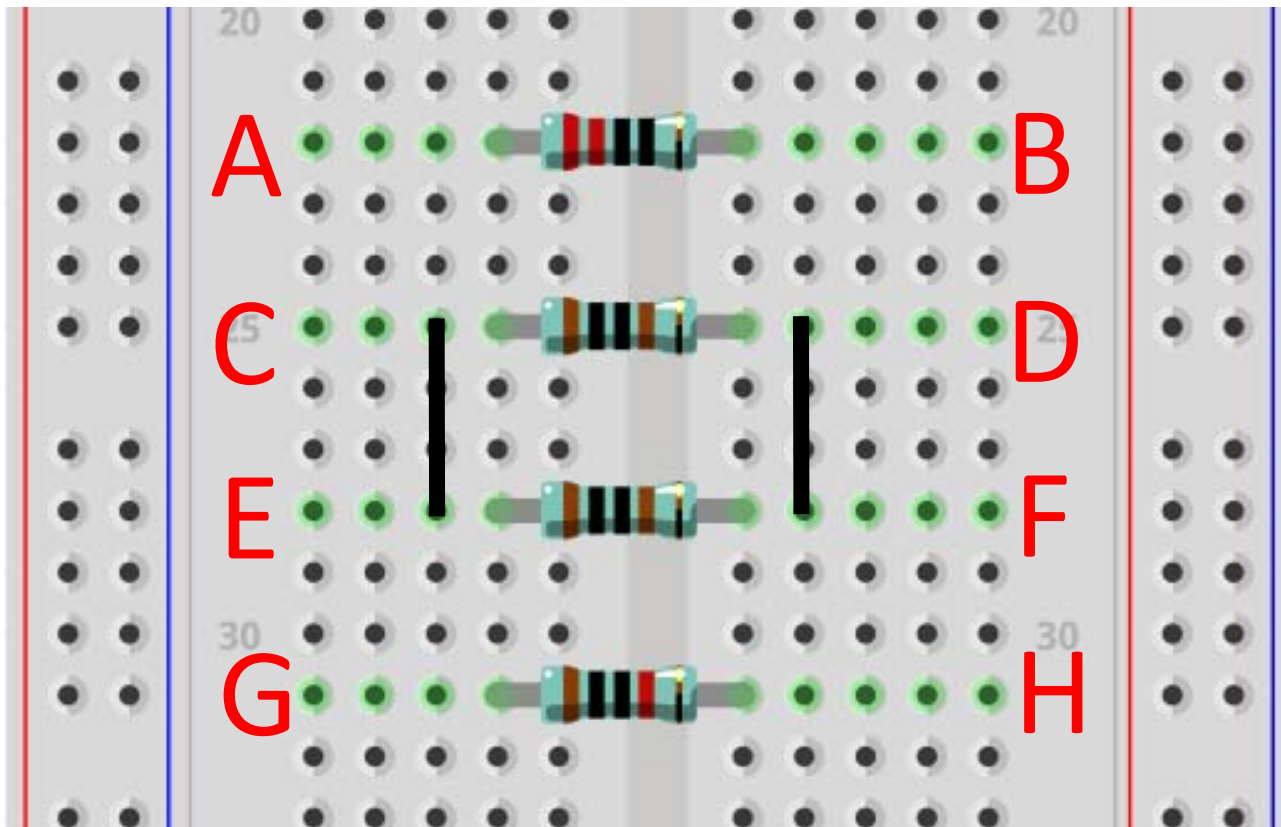
- The 2 middle  $1k\Omega$  resistors are said to be in Parallel



# A LITTLE MORE CHALLENGING EXAMPLE

❖ Consider the simple resistor network below. What's the power of the different values of  $R_L$  ?

$R_L$ (k $\Omega$ )	$I_L$ , Current through $R_L$ (mA)	$V_L$ Voltage at $R_L$ (mV)	$P_L$ Power at $R_L$ (mW)
0.6			
1.2			
1.8			
2.4			2.6
3.0			
3.6			
4.0			

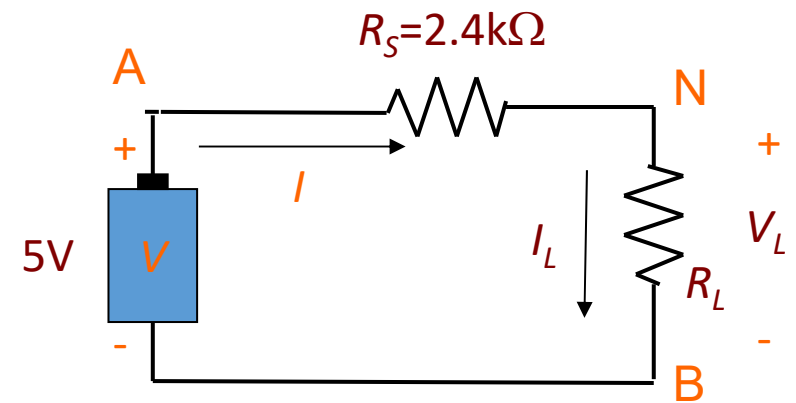

Can you plot the graph Power at  $R_L$  vs  $R_L$  ?

How does the curve look like?